

SCHOOL AMATEUR RADIO CLUB NETWORK®

STEM WORKSHOP - ELECTRONICS PROTOTYPING

- **BUILD A WORKING ELECTRONIC CIRCUIT – FASCINATING TO WATCH!**
- **READ ELECTRONIC COMPONENT SYMBOLS AND CIRCUIT DIAGRAMS**
- **UNDERSTAND DIFFERENT COMPONENT FUNCTIONS AND MARKINGS**
- **VISUALISE HOW ELECTRIC CURRENT FLOWS THROUGH THE CIRCUIT**
- **INCLUDES A REUSABLE PROTOTYPING BOARD AND ALL COMPONENTS**
- **INCLUDES A PRINTED CIRCUIT BOARD FOR HOME CONSTRUCTORS**
- **DOWNLOAD ADDITIONAL WORKSHOP NOTES FOR MORE PROJECTS**
- **DOWNLOAD THE PCB ASSEMBLY BOOK AT www.sarcnet.org**


PROTOTYPING BOARD

DESCRIPTION

PROTOTYPING BOARDS
ARE USED TO CREATE
CIRCUITS OF ELECTRONIC
COMPONENTS WITHOUT
HAVING TO SOLDER THEM
THE COMPONENTS CAN BE
REMOVED AND RESUSED
MANY TIMES

HOLES ARE SPACED 0.1
INCHES APART TO SUIT
MANY TYPES OF
ELECTRONIC
COMPONENTS, EVEN
INTEGRATED CIRCUITS

PHOTOGRAPH

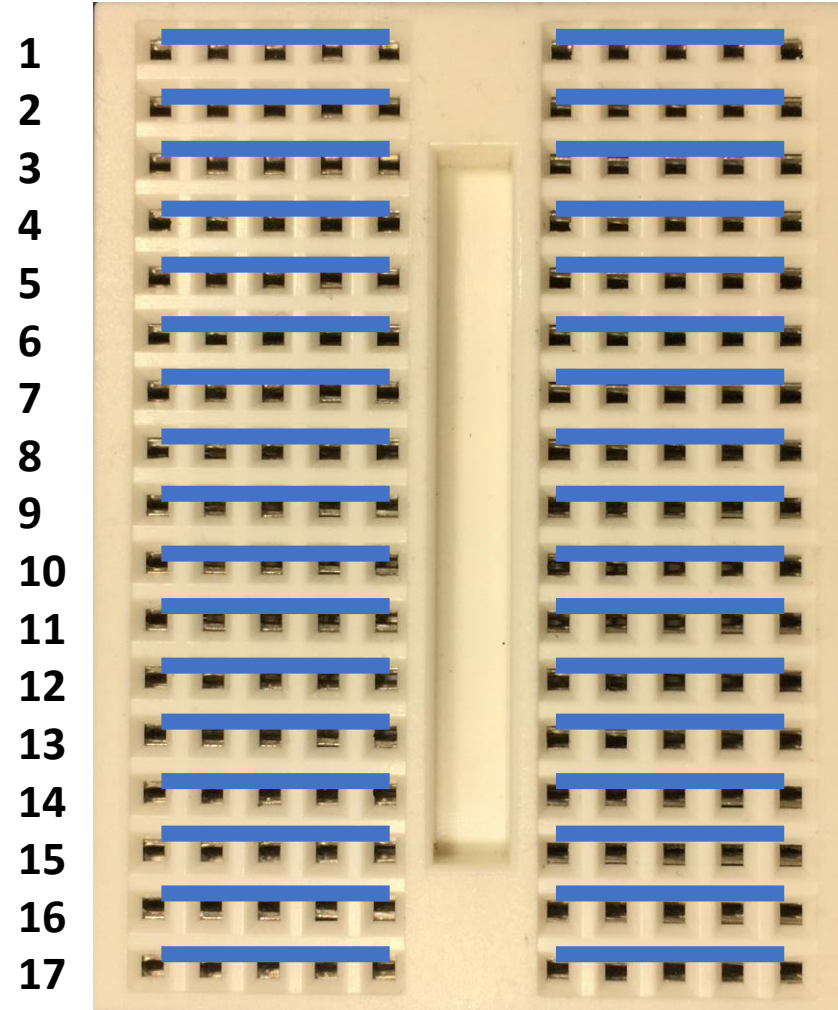

NOTES

17 ROWS BY 10 COLUMNS

170 TIE POINTS IN TOTAL

THE TIE POINTS ON EACH ROW
ARE CONNECTED TOGETHER AS
SHOWN IN BLUE

THE LEFT AND RIGHT ROWS ARE
NOT CONNECTED TOGETHER

PLEASE INSERT COMPONENT
LEADS GENTLY


WIGGLE COMPONENTS SO AS
NOT TO BEND THE LEADS

THE PROTOTYPING BOARD HAS
DOUBLE-SIDED ADHESIVE TAPE

DO NOT REMOVE THE BACKING

WIRE LINKS

SYMBOL AND FUNCTION

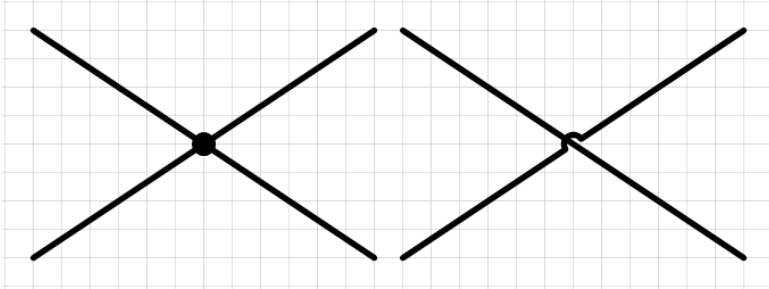

**WIRES CAN BE CONNECTED
OR NOT-CONNECTED AS
SHOWN**

**WIRE LINKS CONNECT
SEPARATE ROWS OF THE
PROTOTYPING BOARD TO
FORM A CIRCUIT**

**TALL LINKS CAN CROSS OVER
OTHER LINKS**

PHOTOGRAPH



NOTES

1 x TALL LINK

1 x WIDE LINK

2 x SHORT LINKS


STEP 1: INSERT WIRE LINKS

WIGGLE THE COMPONENT UNTIL THE LEADS GO INTO THE HOLE EASILY

DO NOT PRESS HARD OR BEND THE LEADS


PRESS BOTH SIDES DOWN TOGETHER

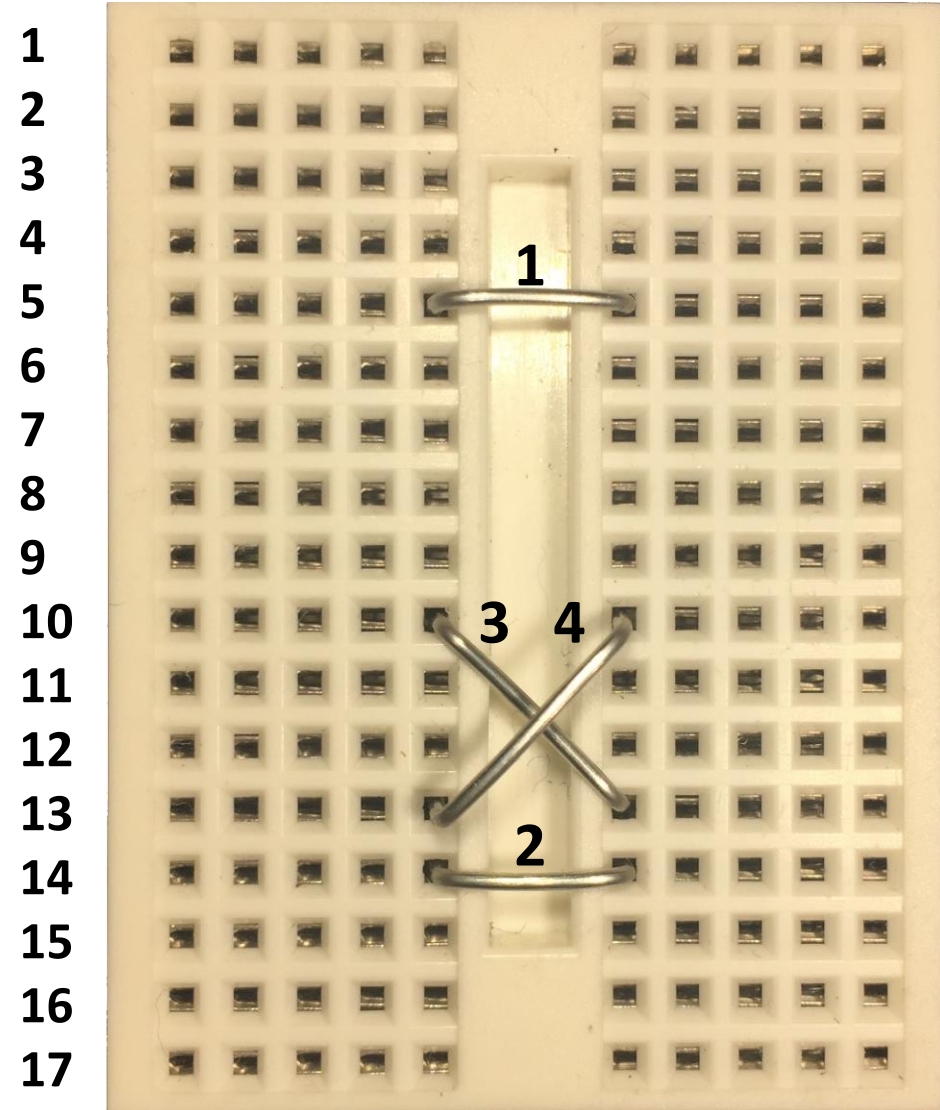1. INSERT A SHORT WIRE LINK ACROSS THE CENTRE COLUMN ON ROW 5
2. INSERT A SHORT WIRE LINK ACROSS THE CENTRE COLUMN ON ROW 14
3. INSERT A WIDE WIRE LINK ACROSS THE CENTRE COLUMN ON THE DIAGONAL FROM ROW 10 TO THE ROW 13
4. INSERT A TALL WIRE LINK ACROSS THE CENTRE COLUMN ON THE DIAGONAL FROM ROW 10 TO THE ROW 13. IT SHOULD NOT TOUCH THE LINK UNDERNEATH.



RESISTORS

SYMBOL AND FUNCTION

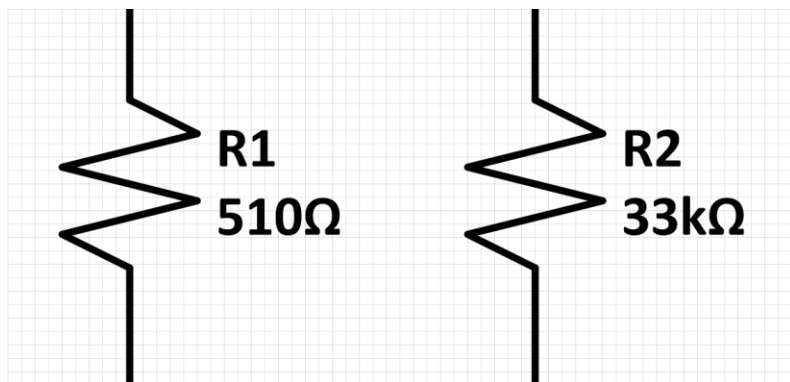


**RESISTORS LIMIT THE FLOW
OF ELECTRIC CURRENT IN A
CIRCUIT TO A SAFE LEVEL
BY CONVERTING THE
EXCESS ENERGY INTO HEAT
RESISTANCE IS MEASURED
IN OHMS (Ω)**

PHOTOGRAPH



NOTES

2 x 510 Ω RESISTORS

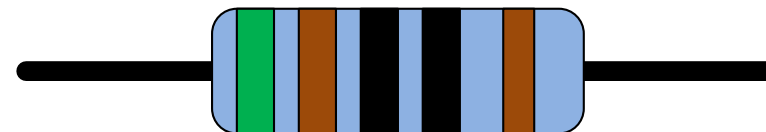

2 x 33 k Ω RESISTORS





RESISTOR COLOUR CODE									
0	1	2	3	4	5	6	7	8	9
BAND 1	BAND 2	BAND 3	BAND 4	BAND 5	VALUE				
DIGIT 1	DIGIT 2	DIGIT 3	# ZEROS	TOL %					
5	1	0	0	1	510 OHM 1%				
3	3	0	2	1	33000 OHM 1%				

STEP 2: INSERT THE RESISTORS

1. INSERT THE SHORT 33 k Ω RESISTORS FROM ROW 5 TO ROW 10 ON EITHER SIDE OF THE TOP LINK. PLACE THE ORANGE BAND AT THE TOP.




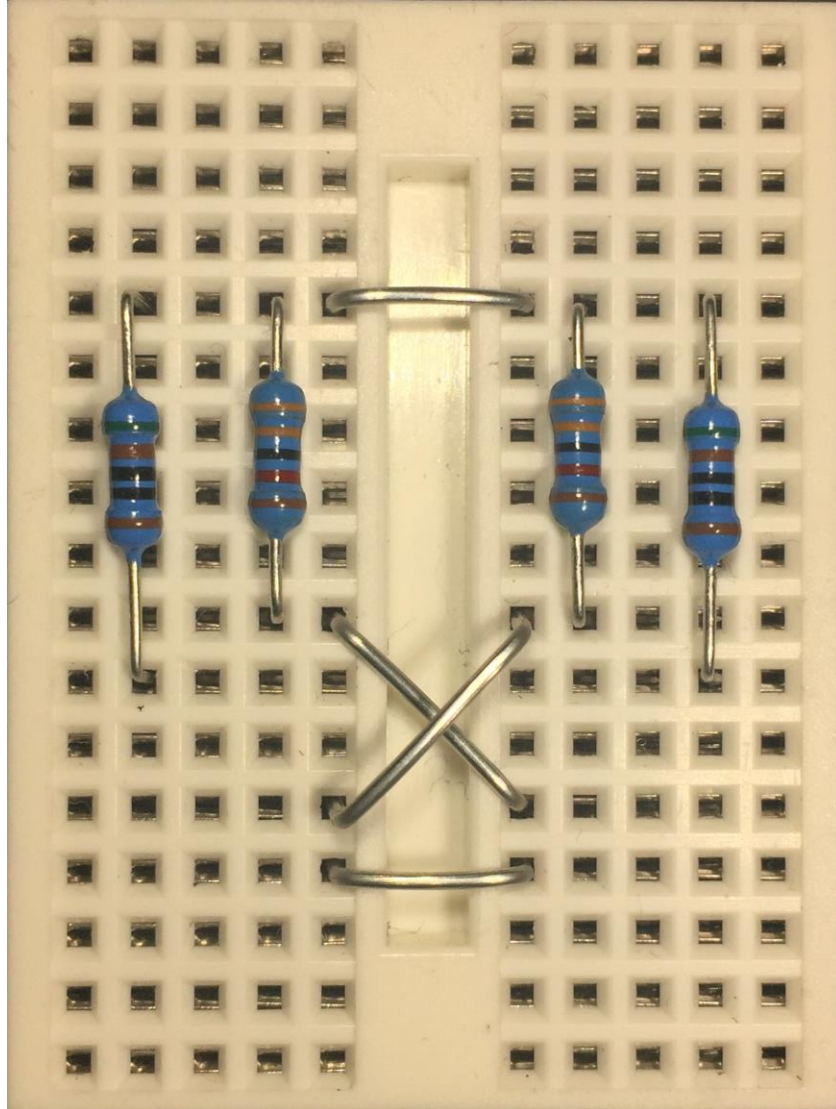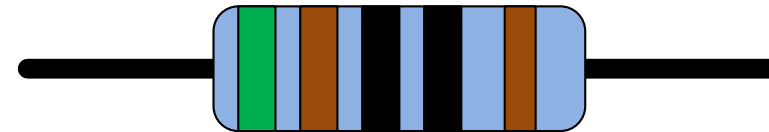2. INSERT THE LONGER 510 Ω RESISTORS FROM ROW 5 TO ROW 11, SEPARATED BY ONE SPACE ON EITHER SIDE OF THE 33 k Ω RESISTORS. PLACE THE GREEN BAND AT THE TOP.




TRANSISTORS

SYMBOL AND FUNCTION

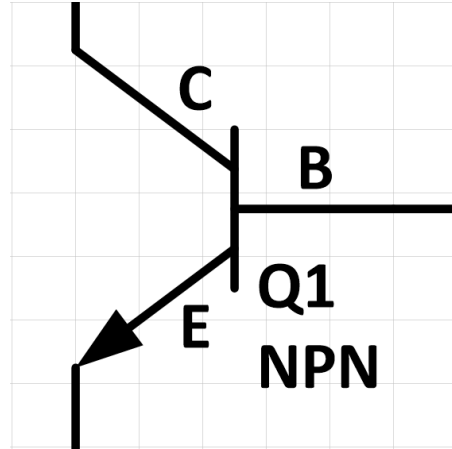

WHEN A VERY SMALL
ELECTRIC CURRENT FLOWS
INTO THE BASE (B) IT
SWITCHES ON A MUCH
LARGER CURRENT FLOWING
FROM THE COLLECTOR (C) TO
THE EMITTER (E) IN THE
DIRECTION OF THE ARROW

PHOTOGRAPH

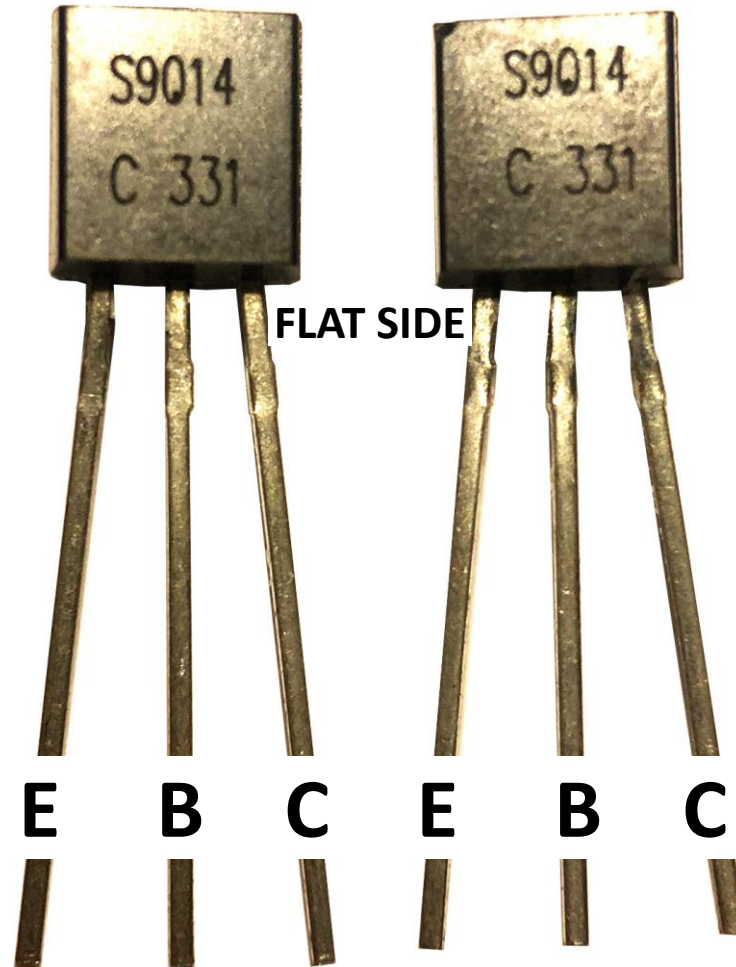


NOTES

2 x NPN TRANSISTORS

SPREAD THE TRANSISTOR
LEADS SLIGHTLY APART AS
SHOWN

STEP 3: INSERT THE TRANSISTORS

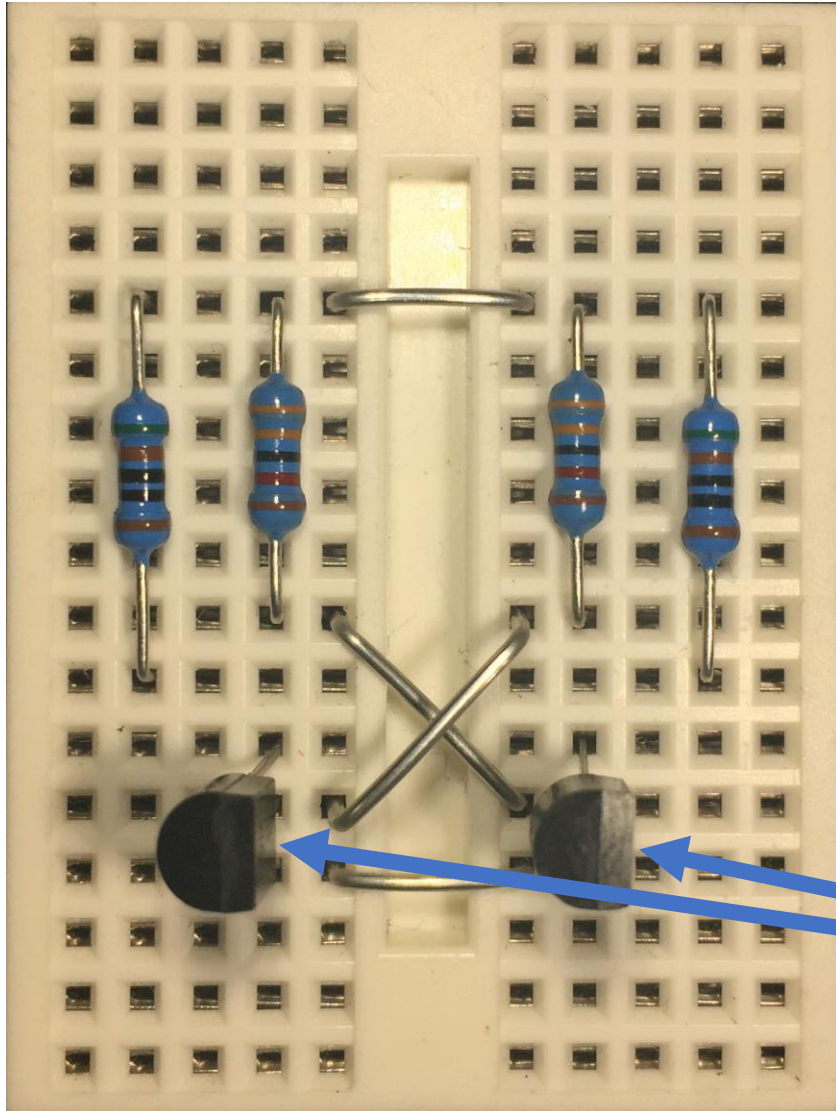
1. INSERT A TRANSISTOR ON EITHER SIDE OF THE LINKS IN ROWS 12, 13 AND 14
2. REMEMBER TO SPREAD THE LEADS AND WIGGLE THE COMPONENT
3. THE FLAT SIDE OF THE TRANSISTORS SHOULD FACE THE RIGHT



FLAT SIDE

CAPACITORS


SYMBOL AND FUNCTION

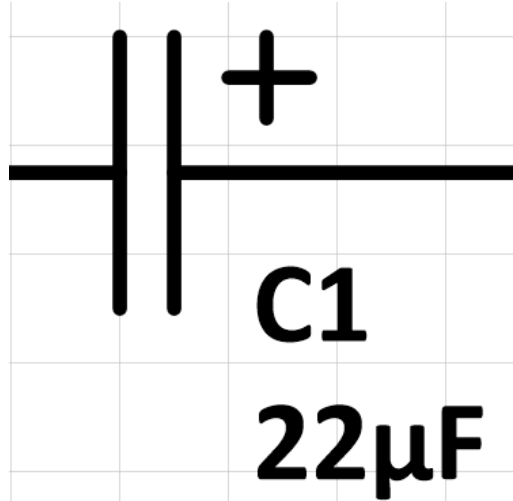

CAPACITORS CAN BE
CHARGED UP AND
DISCHARGED LIKE A TINY
BATTERY

CAPACITANCE IS
MEASURED IN MICRO
FARADS (μ F)

PHOTOGRAPH

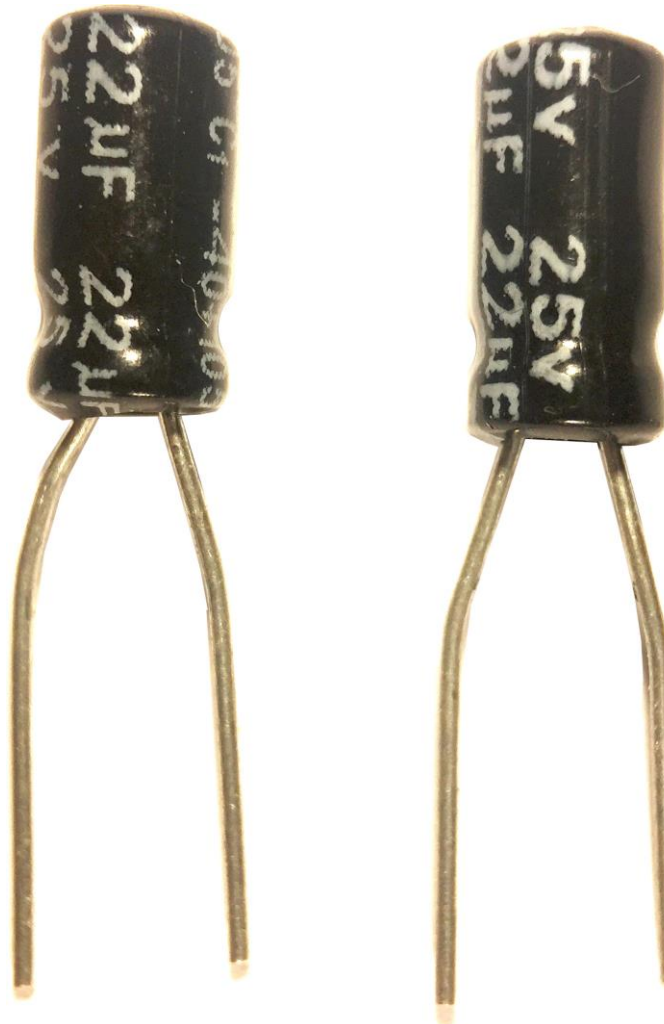

NOTES

2 x 22 μ F CAPACITORS


SPREAD THE CAPACITOR
LEADS SLIGHTLY APART AS
SHOWN

THIS MARK INDICATES THE
NEGATIVE LEAD:




STEP 4: INSERT THE CAPACITORS

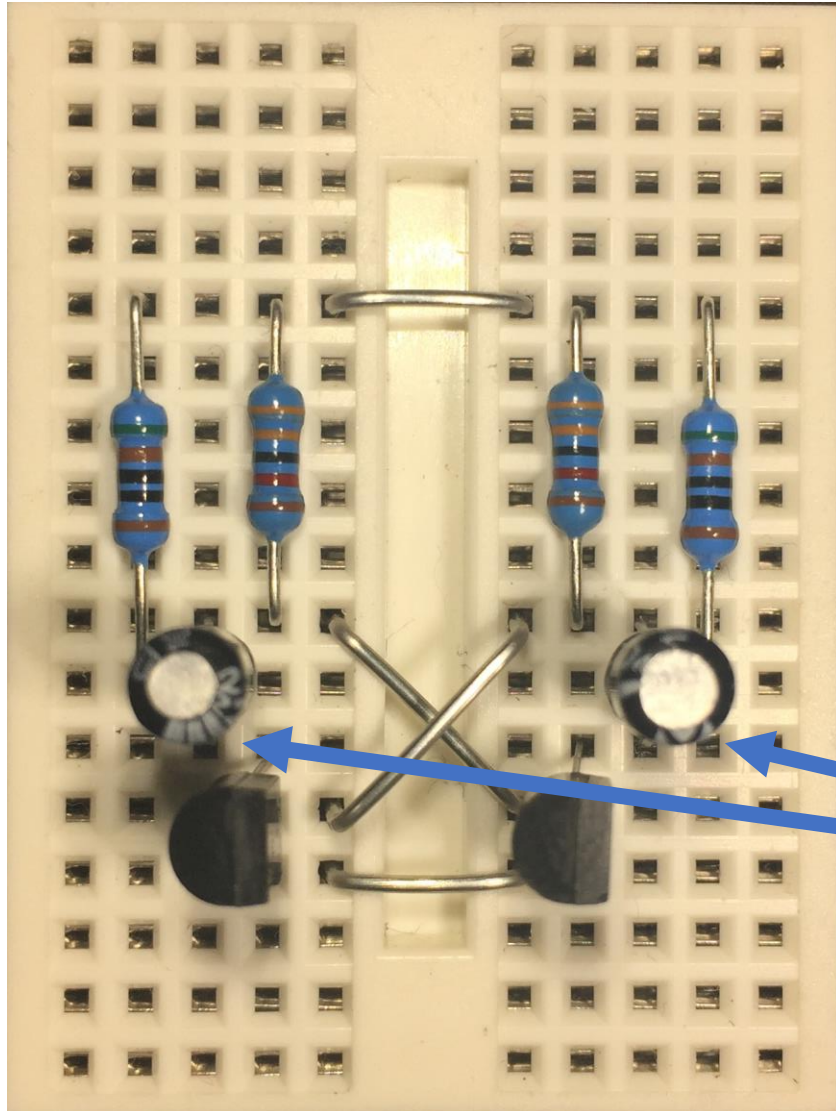1. INSERT THE CAPACITORS ON EITHER SIDE OF THE CENTRE IN THE COLUMN BETWEEN THE RESISTORS
2. THE CAPACITOR LEADS GO INTO ROW 10 AND 12. THERE SHOULD BE ONE ROW SPACE BETWEEN THEM.
3. REMEMBER TO SPREAD THE LEADS AND WIGGLE THE COMPONENT
4. THE NEGATIVE LEAD OF THE CAPACITOR SHOULD BE CONNECTED TO ROW 12




LIGHT EMITTING DIODES (LEDs)

SYMBOL AND FUNCTION

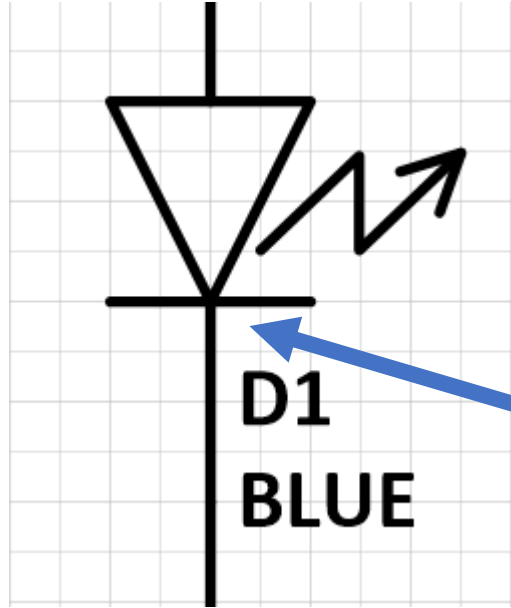

LIGHT EMITTING DIODES
CONVERT ELECTRIC CURRENT
DIRECTLY INTO LIGHT

PHOTOGRAPH

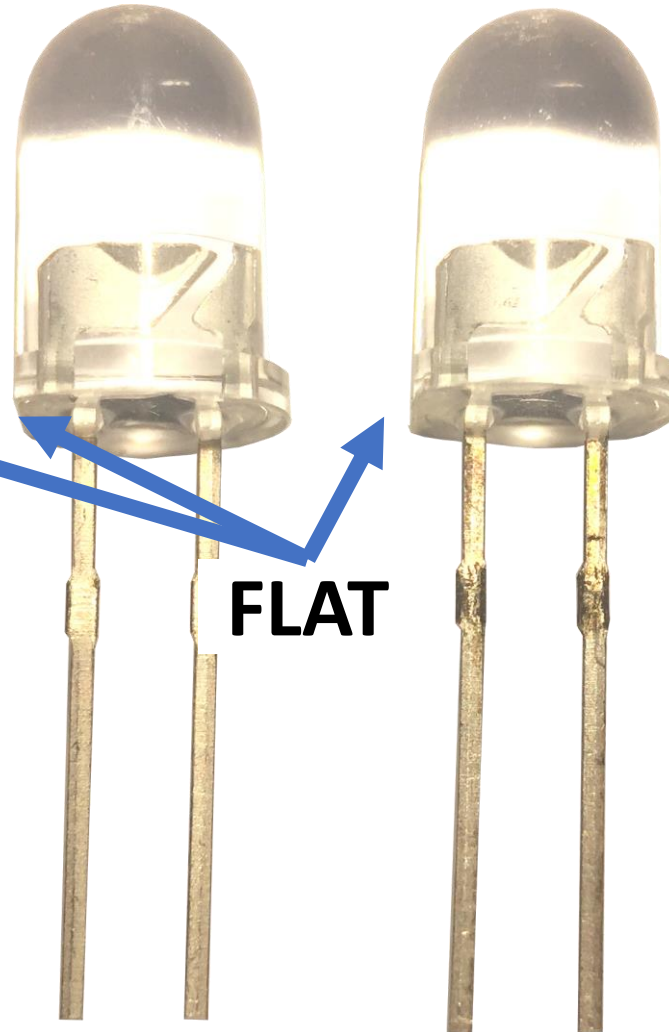

NOTES

2 x BLUE LEDs


THE FLAT SIDE OF THE LED
INDICATES THE NEGATIVE
LEAD

SEE INTERNAL "POST" AND
"ANVIL" STRUCTURE

THE "POST" IS THE
POSITIVE LEAD

STEP 5: INSERT THE LEDs

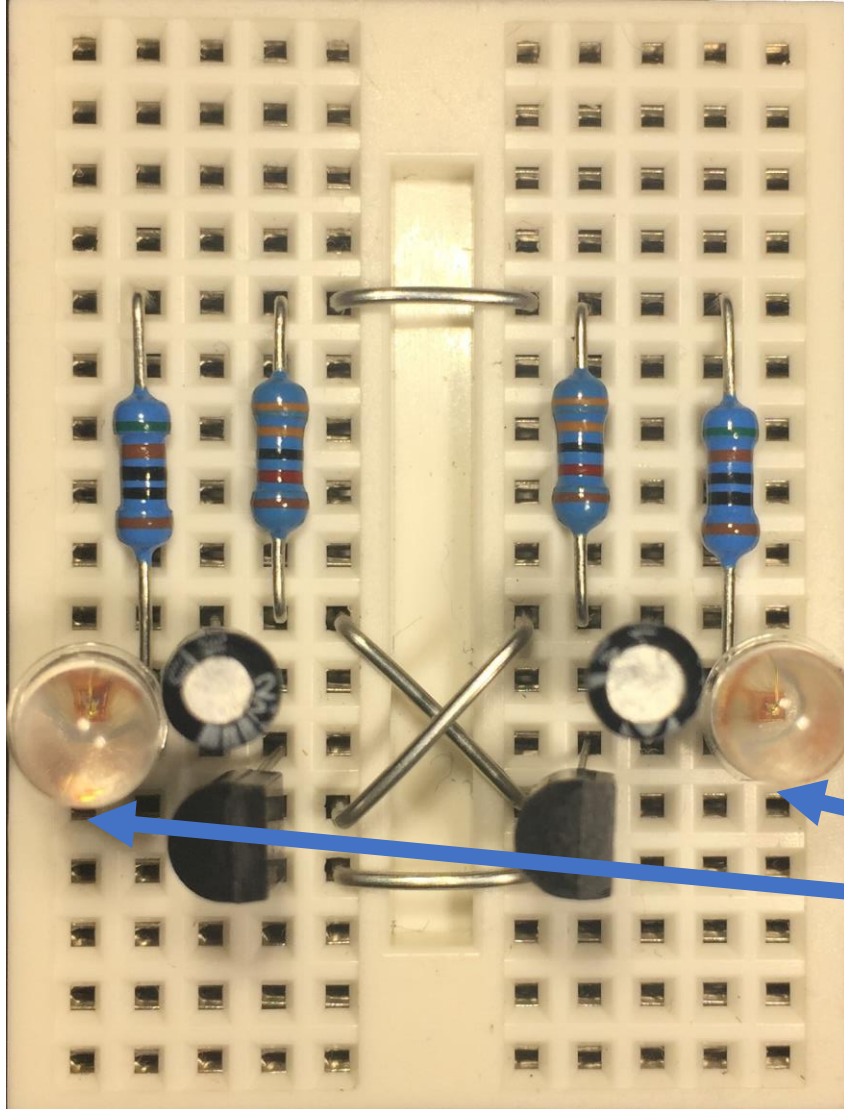
1. INSERT THE LEDs ON THE OUTSIDE OF THE 510 Ω RESISTORS IN ROWS 11 AND 12.
2. THE FLAT SIDE OF THE LED SHOULD BE AT THE BOTTOM



FLAT SIDE

BATTERY AND SWITCH

SYMBOL AND FUNCTION

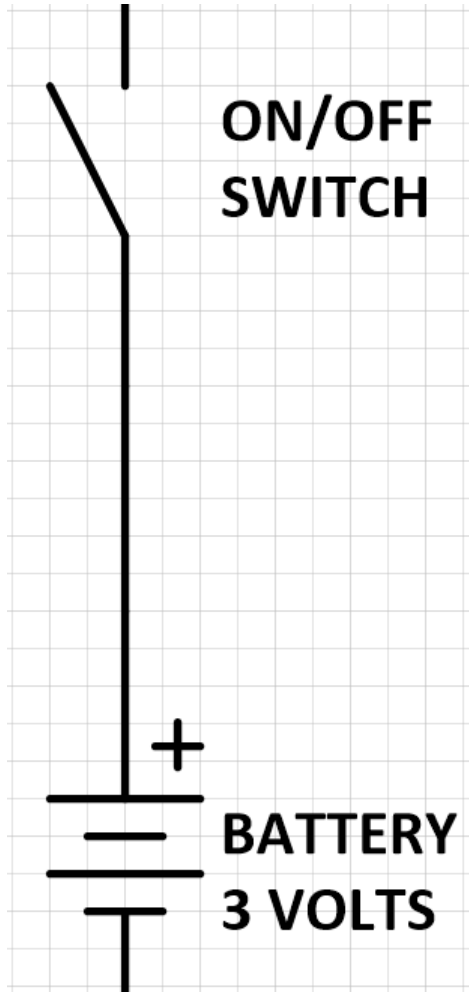

THE BATTERY
POWERS THE
CIRCUIT

TWO 1.5 VOLT
AA CELLS ARE
CONNECTED IN
SERIES TO
PRODUCE 3
VOLTS

THE SWITCH
CONTROLS THE
FLOW OF
ELECTRIC
CURRENT INTO
THE CIRCUIT.

PHOTOGRAPH



NOTES

THE BATTERY WILL BE PROVIDED
FOR TESTING YOUR CIRCUIT AT THE
END OF THE WORKSHOP


**ENSURE THE SWITCH IS OFF AND
REMOVE BATTERIES WHEN NOT IN
USE.**

**NEVER CONNECT THE WIRES
TOGETHER**

THE **RED** WIRE IS POSITIVE
THE BLACK WIRE IS NEGATIVE

AA CELLS ARE NOT INCLUDED

STEP 6: CONNECT THE BATTERY

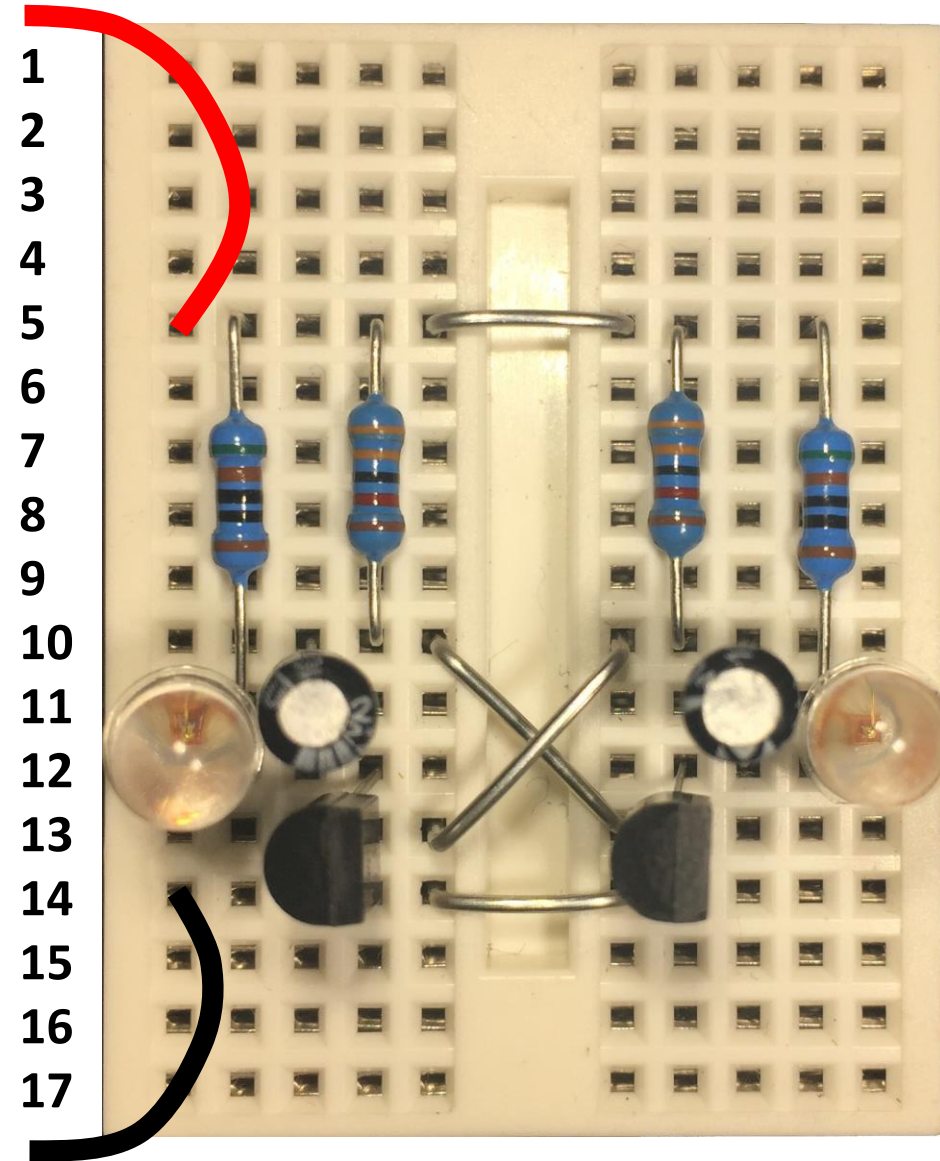

1. CHECK THE ASSEMBLY ONE MORE TIME. ENSURE ALL COMPONENTS ARE IN THE RIGHT PLACE AND ORIENTED CORRECTLY.
2. MAKE SURE THE BATTERY SWITCH IS OFF

WARNING: IF YOU CONNECT THE BATTERY LEADS TOGETHER AND TURN THE SWITCH ON, THE BATTERY COULD GET HOT AND MAY START A FIRE. ALWAYS REMOVE THE AA CELLS FROM THE BATTERY HOLDER WHEN NOT IN USE.

4. CONNECT THE **RED** LEAD OF THE BATTERY TO ROW 5.
5. CONNECT THE BACK LEAD OF THE BATTERY TO ROW 14
6. TURN THE SWITCH ON AND YOUR LEDs SHOULD FLASH

PRINTED CIRCUIT BOARD

DESCRIPTION


**PRINTED CIRCUIT BOARDS (PCBs)
ARE USED TO CREATE CIRCUITS
OF ELECTRONIC COMPONENTS
BY SOLDERING THE COMPONENT
LEADS TO SOLDER PADS**

**COPPER PCB TRACKS CONNECT
THE COMPONENT LEADS TO
FORM A CIRCUIT**

**COMPONENTS CANNOT BE
REMOVED VERY EASILY**

**THE PCB ASSEMBLY IS MORE
STABLE AND PERMANENT**

PHOTOGRAPH

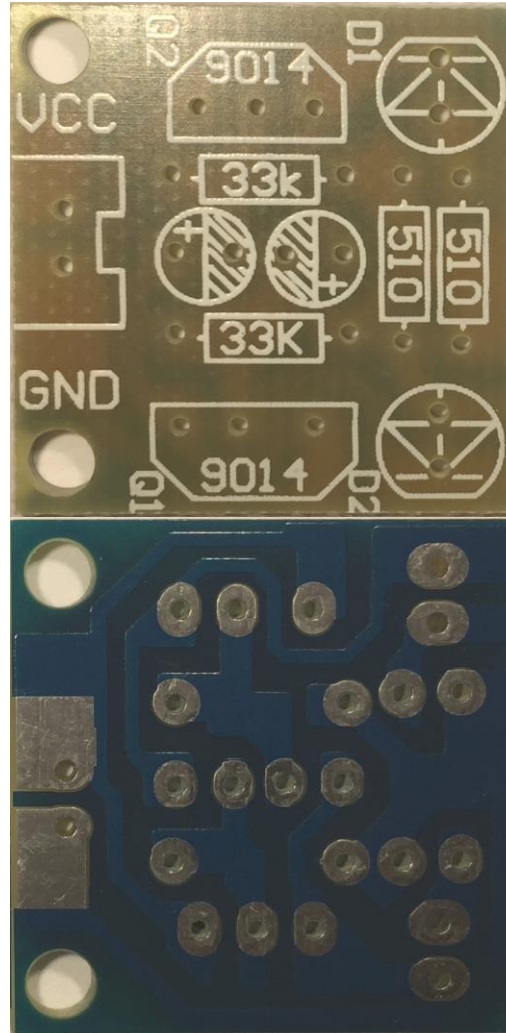

NOTES

**HOLES IN THE PCB PERMIT
COMPONENT LEADS TO FIT
THROUGH THE BOARD**

**THE FRONT OF THE PCB HAS A
WHITE, SILK-SCREENED PATTERN
SHOWING WHERE EACH
COMPONENT IS MOUNTED AND
ITS CORRECT ORIENTATION**

**THE BACK OF THE PCB HAS A
BLUE SOLDER MASK TO ENSURE
THAT SOLDER ONLY FLOWS ON
THE SOLDER PADS**




FLASHER

HOW IT WORKS



THE ELECTRONIC COMPONENTS ARE REPRESENTED BY SYMBOLS IN THE CIRCUIT DIAGRAM SHOWN BELOW. EACH COMPONENT HAS A DESIGNATOR AND A VALUE. THEY ARE CONNECTED BY BLACK LINES REPRESENTING WIRES. DOTS SHOW WHERE TWO WIRES ARE CONNECTED. EACH COMPONENT HAS A SPECIAL FUNCTION: TWO 1.5 VOLT AA CELLS CONNECTED IN SERIES PRODUCE 3 VOLTS TO POWER THE CIRCUIT. AN ON/OFF SWITCH CONTROLS THE CURRENT INTO THE CIRCUIT. RESISTORS LIMIT THE CURRENT THAT CAN FLOW IN VARIOUS PARTS OF THE CIRCUIT. CAPACITORS CAN BE CHARGED AND DISCHARGED. LIGHT EMITTING DIODES (LEDs) CONVERT CURRENT DIRECTLY INTO LIGHT. TRANSISTORS WORK LIKE AN ON/OFF SWITCH, CONTROLLED BY A SMALL CURRENT FLOWING INTO THEIR BASE (B) CONNECTIONS. WHEN THE SWITCH IS OFF, NO CURRENT FLOWS IN THE CIRCUIT. THE TRANSISTORS AND LEDs ARE TURNED OFF AND THE CAPACITORS ARE DISCHARGED. WHEN THE SWITCH IS FIRST TURNED ON, CURRENT FLOWS DOWN THROUGH R2 INTO Q2 AND R3 INTO Q1. YOU CAN TRACE IT WITH YOUR FINGER. IT IS INITIALLY A RACE TO SEE WHICH TRANSISTOR WILL TURN ON FIRST. SUPPOSE Q1 TURNS ON FIRST. CURRENT WILL FLOW THROUGH R1 AND D1 INTO THE COLLECTOR (C) OF Q1 AND THEN OUT OF ITS EMMITER (E) IN THE DIRECTION OF THE ARROW. R1 LIMITS THE CURRENT THROUGH D1 TO A SAFE VALUE. WHEN Q1 TURNS ON, C1 BEGINS TO CHARGE UP THROUGH R2. Q2 WILL NOT TURN ON UNTIL C1 IS CHARGED. THIS TAKES SOME TIME DEPENDING ON THE VALUES OF R2 AND C1. WHEN C1 IS CHARGED, Q2 TURNS ON. CURRENT FLOWS THROUGH R4, D2 AND Q2, TURNING ON D2 FOR THE FIRST TIME. WHEN Q2 TURNS ON, IT DIVERTS THE CURRENT FLOWING INTO THE BASE OF Q1 FROM R3 TO CHARGE UP C2 INSTEAD. THIS CAUSES Q1 AND D1 TO TURN OFF IMMEDIATELY. THE PROCESS CONTINUES WITH C1 AND C2 BEING CHARGED AND DISCHARGED BY Q1 AND Q2 AND THE LEDs TURNING ON AND OFF ALTERNATELY. THIS FAMOUS CIRCUIT IS CALLED AN "ASTABLE MULTIVIBRATOR". DOWNLOAD MORE WORKSHOP NOTES AT WWW.SARCNET.ORG/WORKSHOPS.HTML.

PARTS LIST

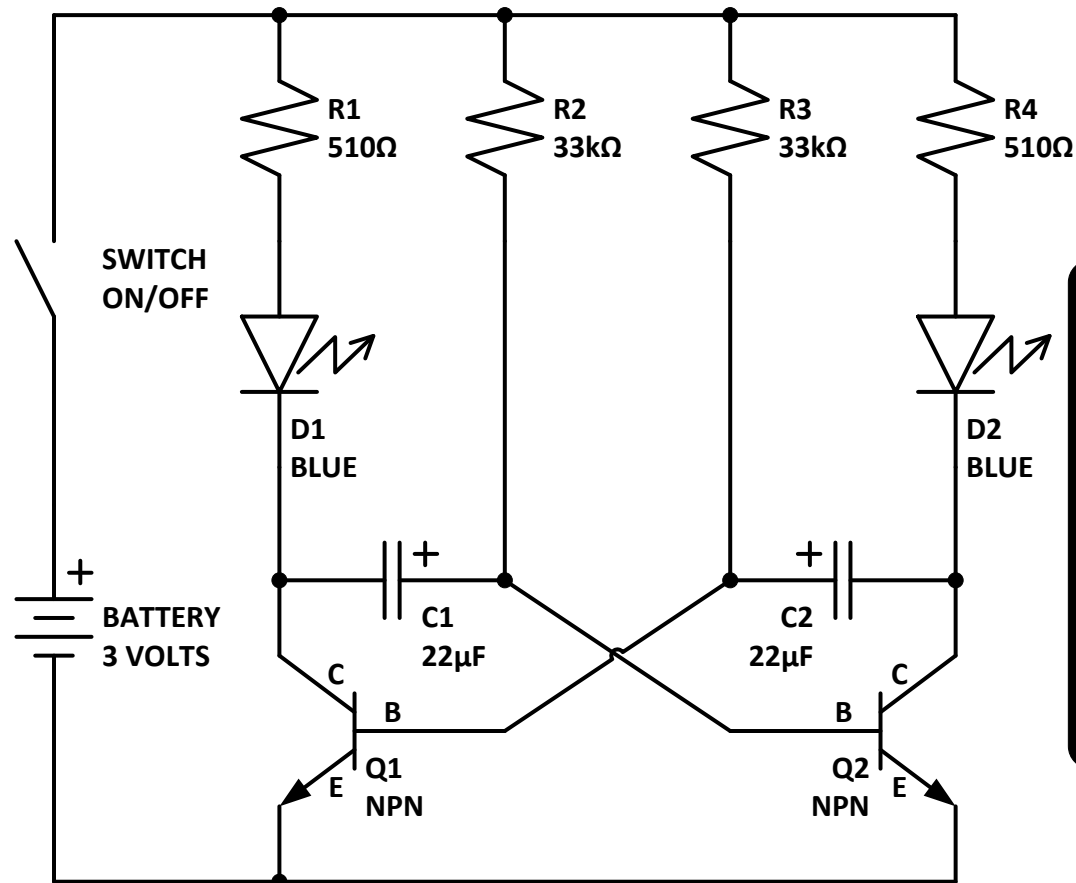- 1 - 3V BATTERY HOLDER WITH SWITCH
- 1 - PROTOTYPING BOARD - 170 TIE POINTS
- 2 - GENERAL PURPOSE NPN TRANSISTOR
- 2 - LIGHT EMITTING DIODE (BLUE)
- 2 - 22 μ F ELECTROLYTIC CAPACITOR
- 2 - 510 Ω 1/4W RESISTOR
- 2 - 33k Ω 1/4W RESISTOR
- 2 - 0.3" WIRE LINK
- 1 - 0.4" WIRE LINK
- 1 - 0.4" WIRE LINK (TALL)




CIRCUIT SCHEMATIC DIAGRAM

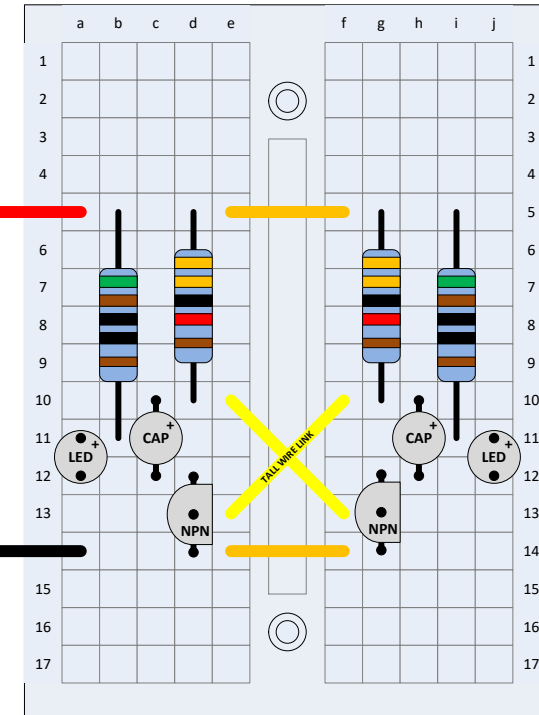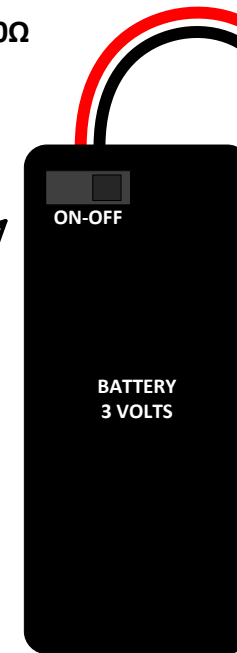

RESISTOR COLOUR CODE					
0	1	2	3	4	5
6	7	8	9		
BAND 1	BAND 2	BAND 3	BAND 4	BAND 5	VALUE
DIGIT 1	DIGIT 2	DIGIT 3	# ZEROS	TOL %	
5	1	0	0	1	510 OHM 1%
3	3	0	2	1	33000 OHM 1%


PROTOTYPE BOARD LAYOUT

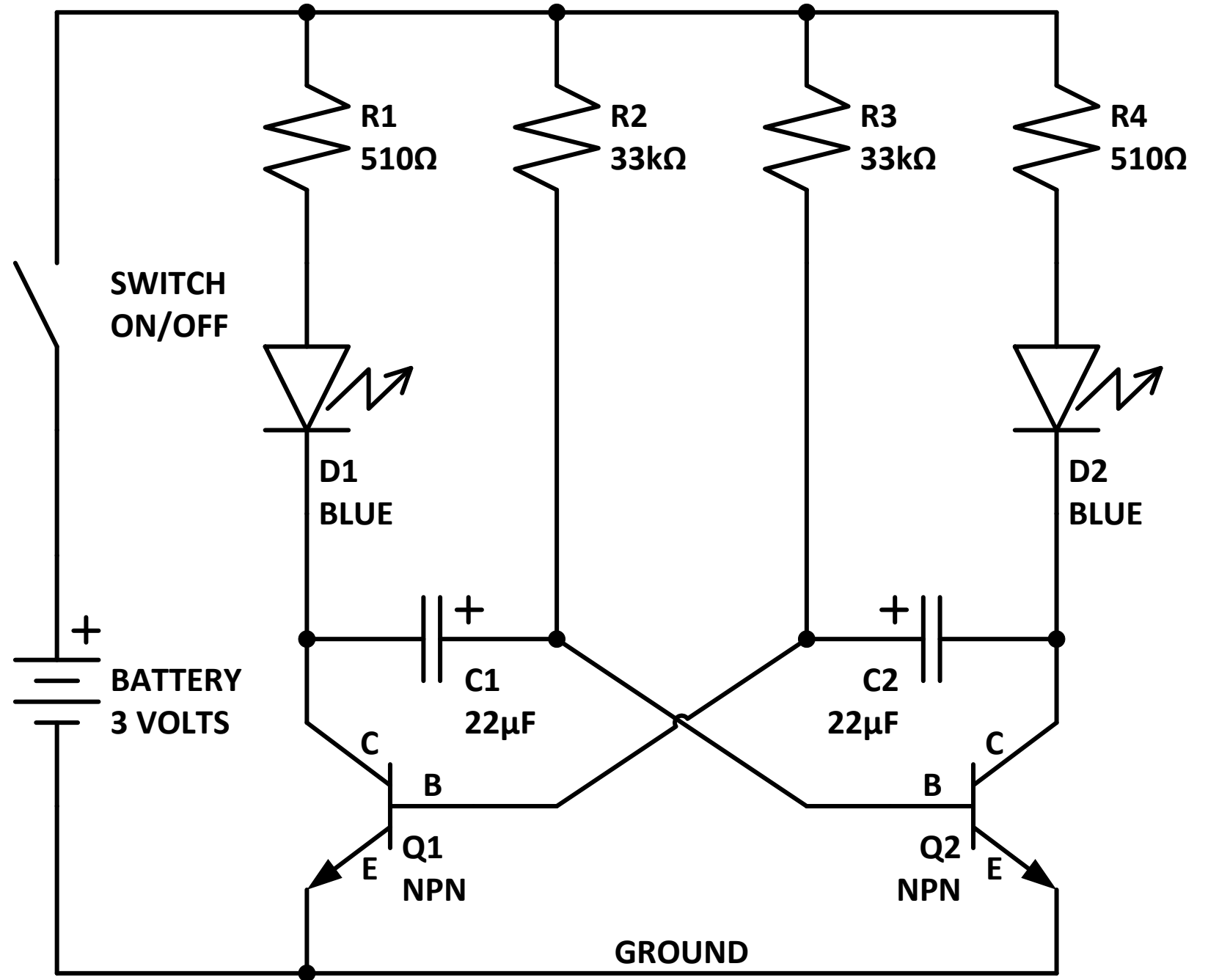The switch is off, so no current flows from the battery into the circuit. The Transistors Q1 and Q2 are both off, so no current flows from their Collectors (C) to their Emitters (E). The Capacitors C1 and C2 are both discharged, so there is no voltage across them.




The wire at the bottom of this circuit is called GROUND for reference.

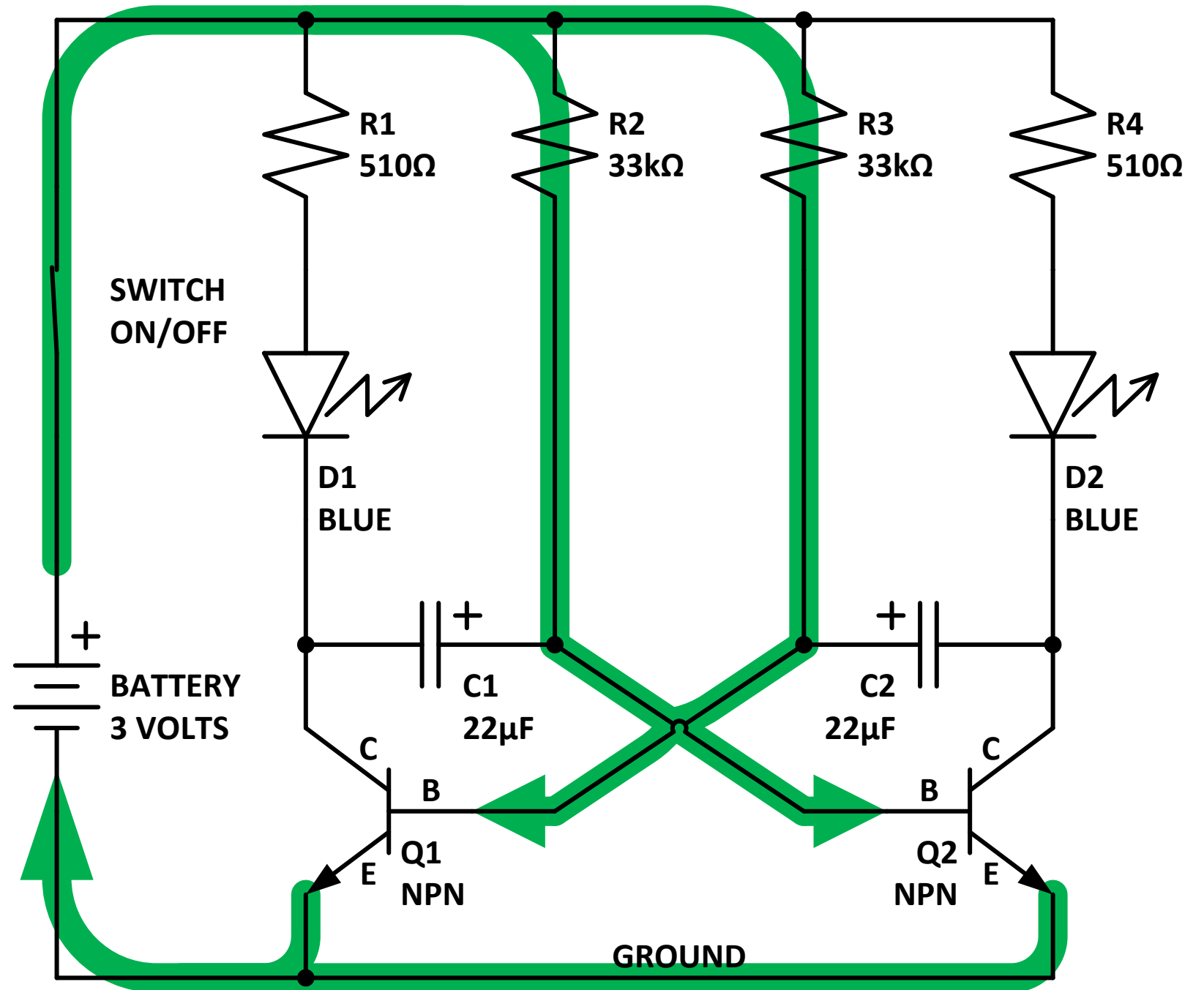
The switch is on. Current flows through resistors R2 and R3 into the Base of Q1 and Q2, down to GROUND and back to the battery. One of the transistors will turn on first. Which one? The fastest depends on minor variations in component parameters. It will be a race...



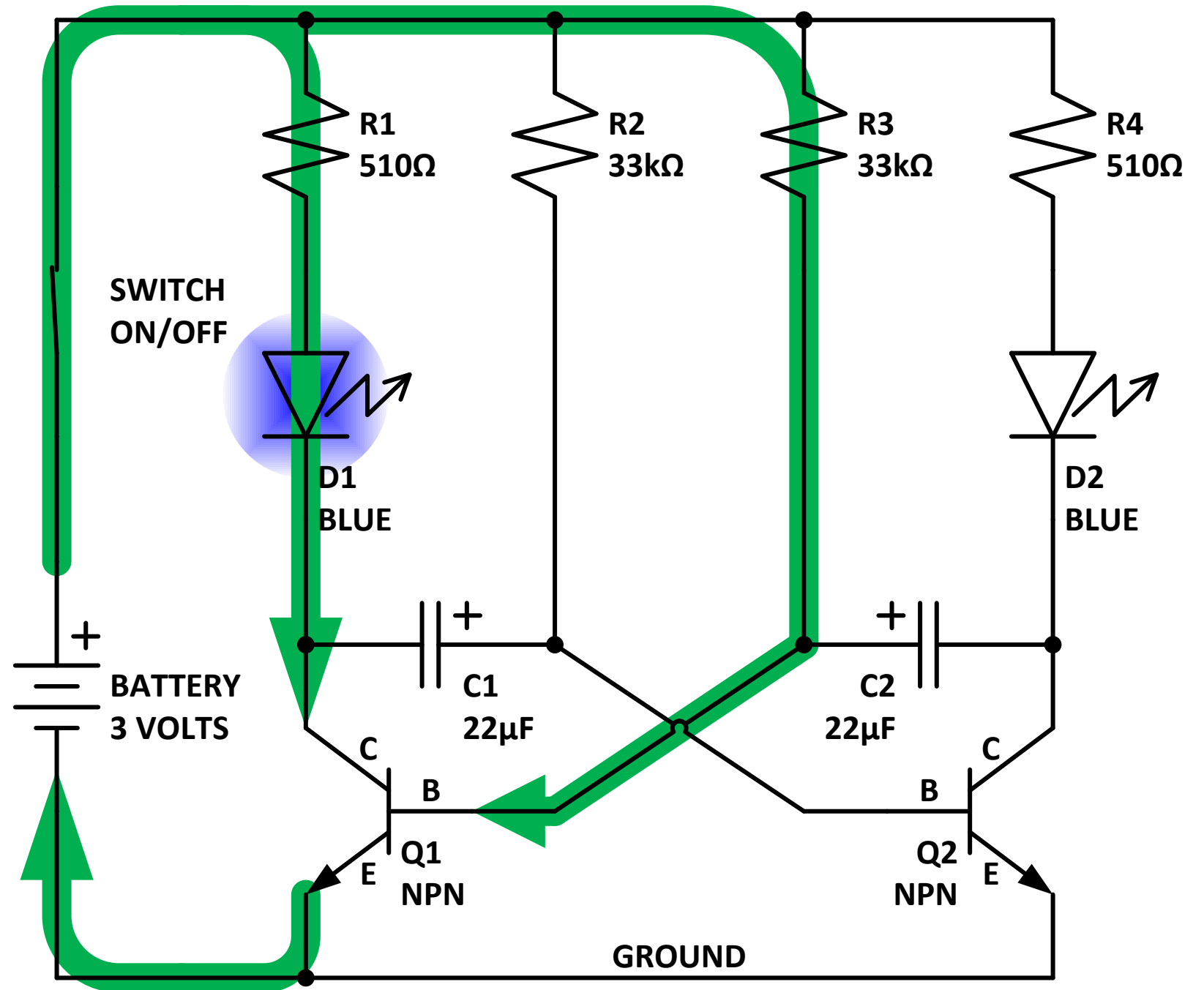
Q1 was the fastest and has turned on first! Current now flows through R1 and LED D1 into the Collector and out of the Emitter of Q1. D1 now emits light. But why doesn't Q2 also turn on as well? Wait and see...




When Q1 turned on it also connected D1 and Capacitor C1 to GROUND. C1 was initially discharged. Since the voltage across a discharged capacitor must be zero, the Positive (+) side of C1 and the Base of Q2 were also pulled down to GROUND. Q2 was therefore switched off when Q1 turned on. However, C1 is now charging through R2. The time it takes for C1 to charge depends on the values of R2 and C1. So, what happens when C1 is charged?...

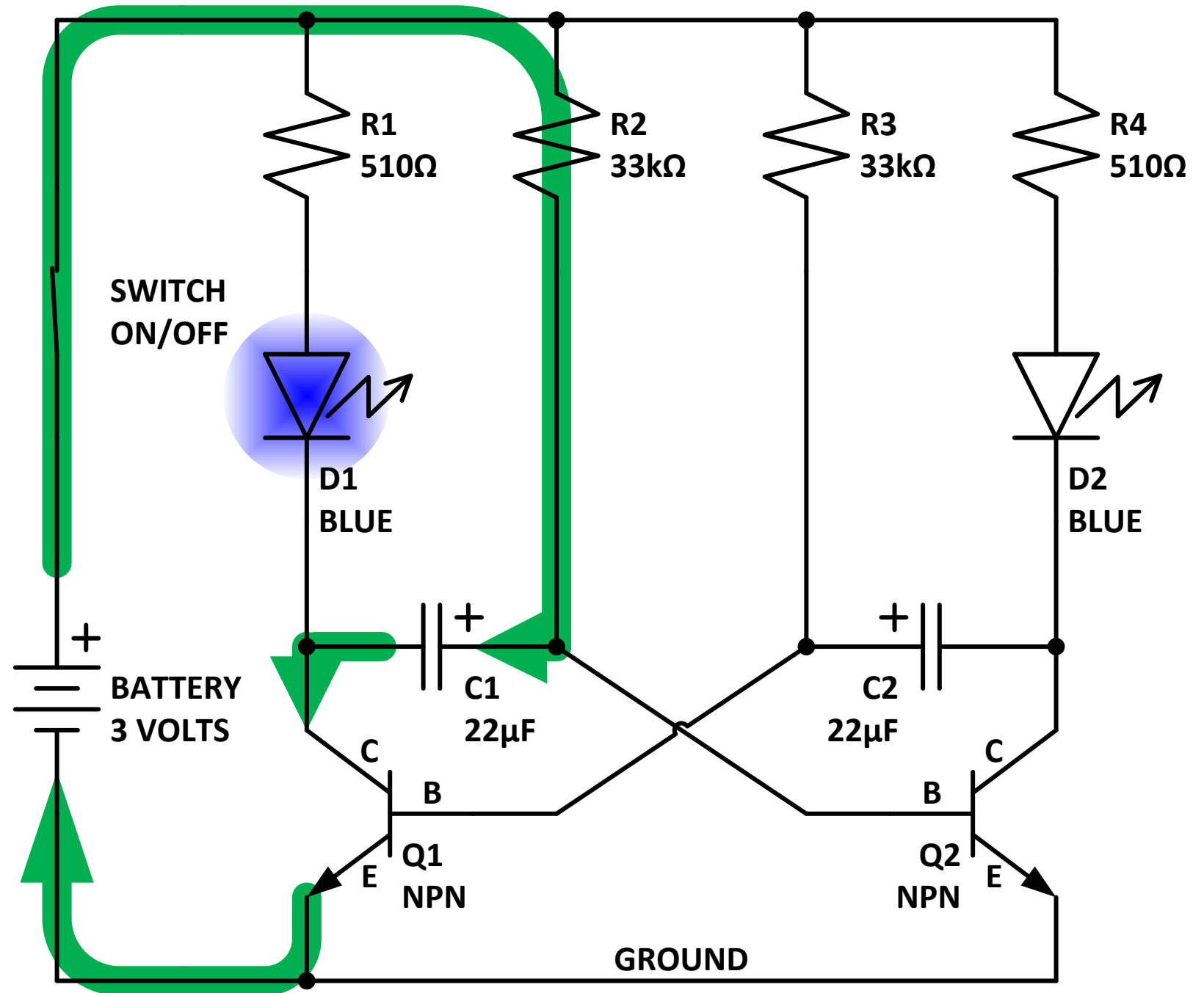

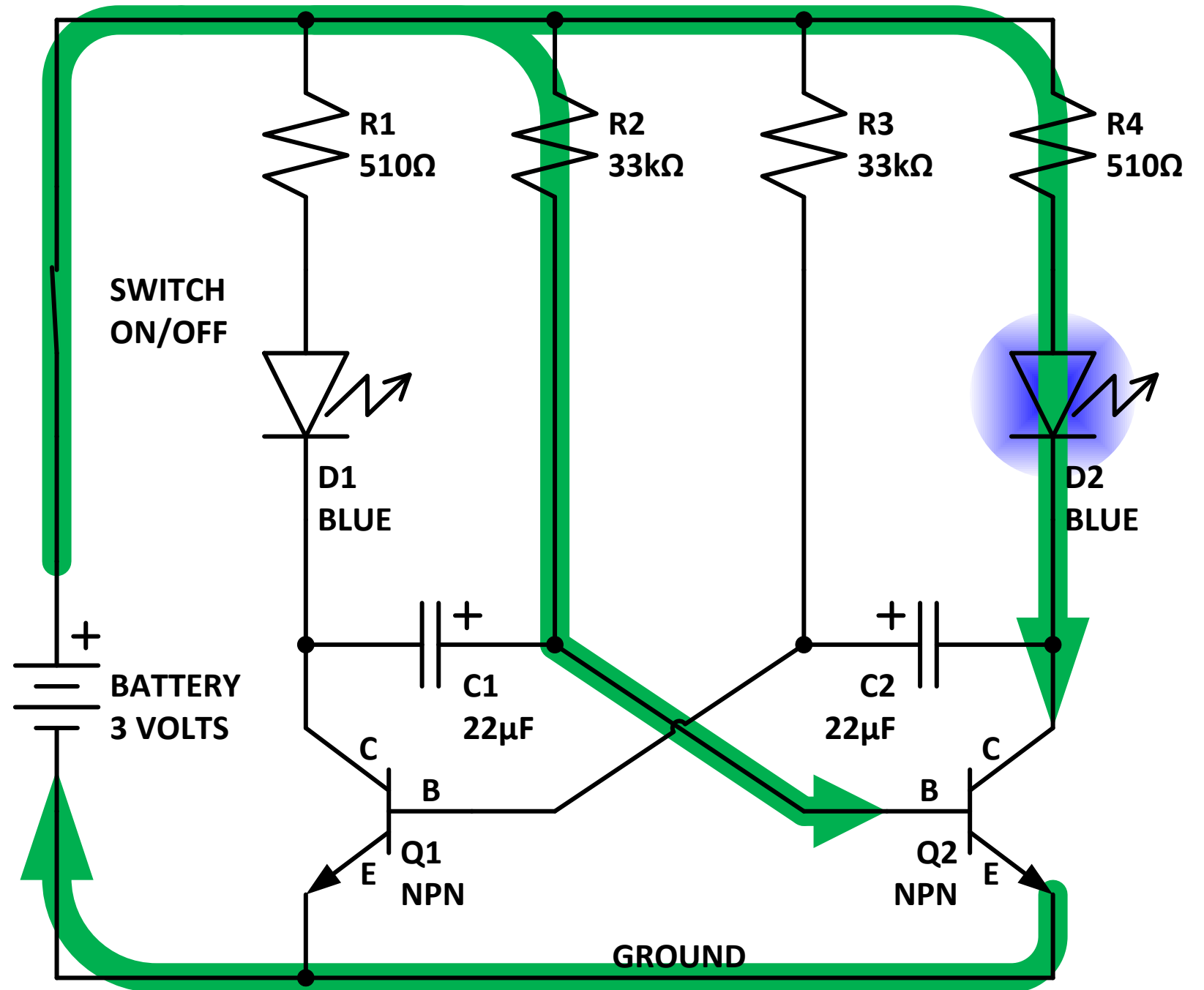
C1 has now been charged through R2. So current flows into the Base of Q2 and it turns on. D2 now emits light. But what makes Q1 turn off?...




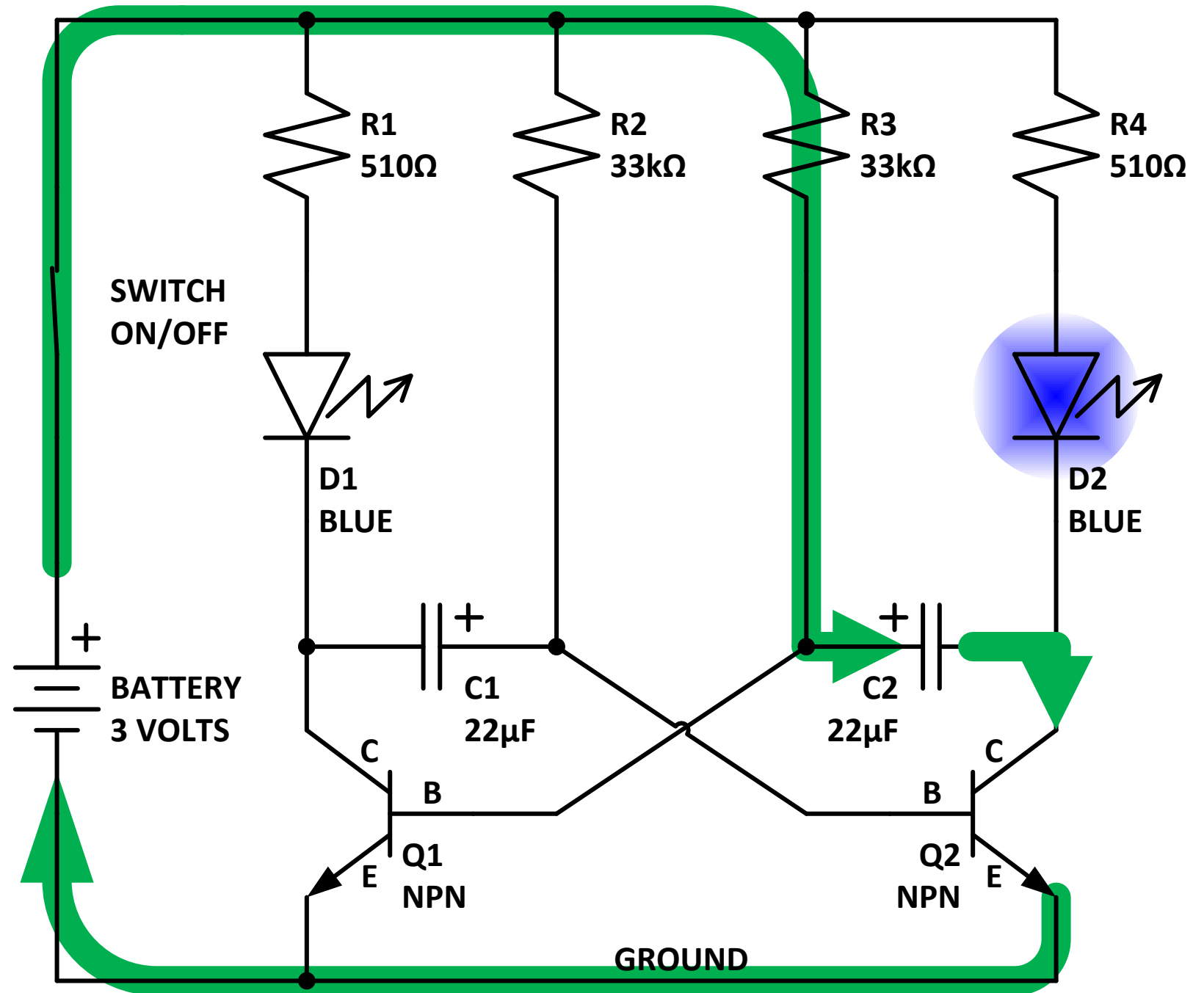C2 was initially discharged when Q2 turned on. Since the voltage across a discharged capacitor must be zero, the Positive (+) side of C2 and the Base of Q1 were also pulled down to GROUND. So Q1 switches off. D1 stops emitting light. C1 discharges into the Base of Q2 and C2 is now charging through R3.



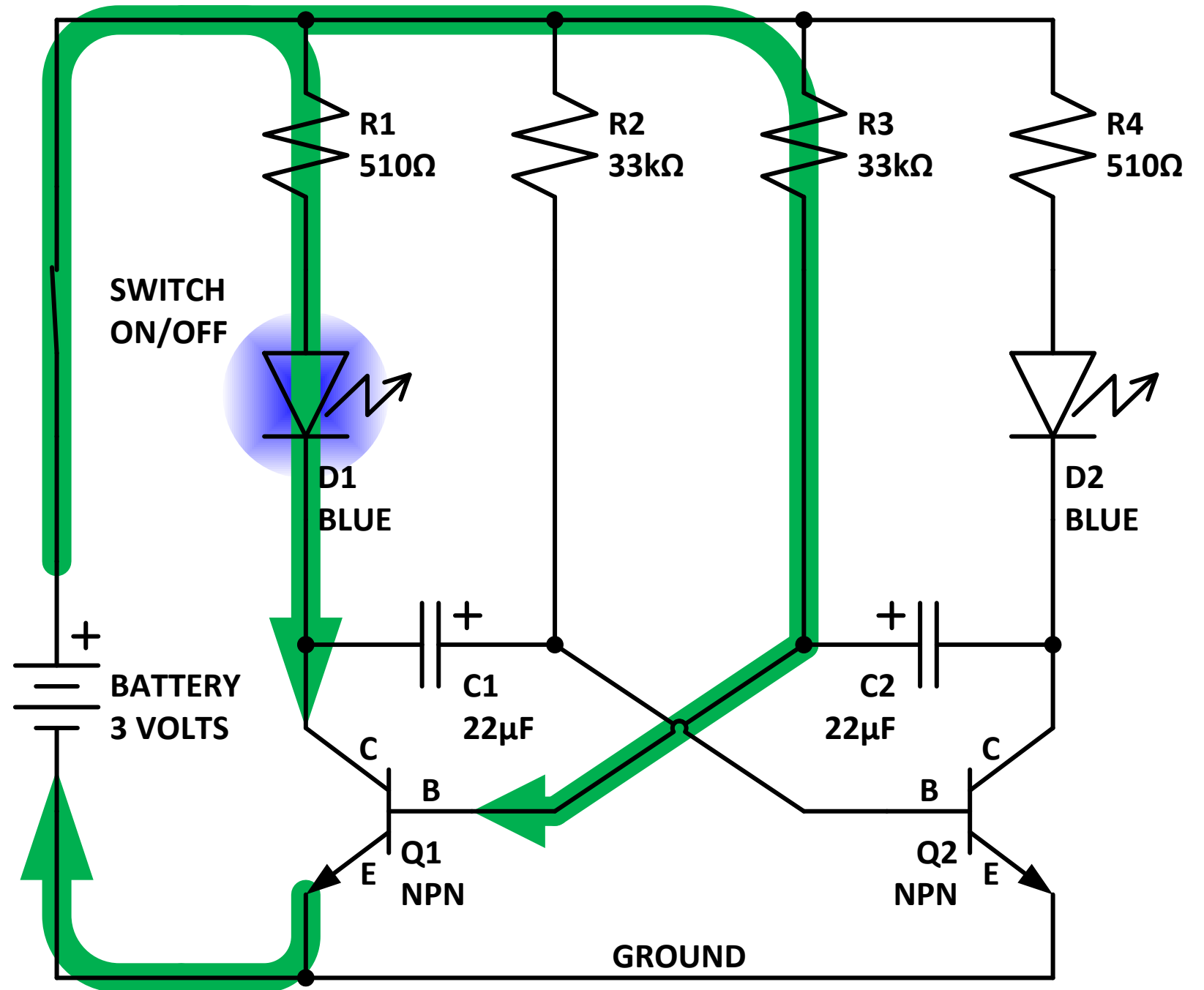When C2 is charged, current flows through R1 and LED D1 into the Collector and out of the Emitter of Q1. The process starts again. The circuit is in fact oscillating like children on a seesaw or teeter-totter. The frequency of oscillation depends mainly in the values of R2(R3) and C1(C2).



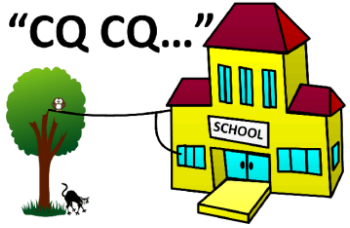

SCHOOL AMATEUR RADIO CLUB NETWORK®

STEM WORKSHOP - ELECTRONICS PROTOTYPING

- **WE HOPE YOU HAD FUN CREATING YOUR OWN ELECTRONIC CIRCUIT**
- **IMAGINE BUILDING YOUR OWN ELECTRONICS KITS AT HOME!**
- **IF YOU HAVE ANY QUESTIONS PLEASE ASK NOW**
- **DON'T FORGET TO VISIT www.sarcnet.org/workshops.html**
- **DOWNLOAD THESE SLIDES AND ALL WORKSHOP NOTES THERE**
- **HOME CONSTRUCTORS CAN DOWNLOAD THE PCB ASSEMBLY BOOK**